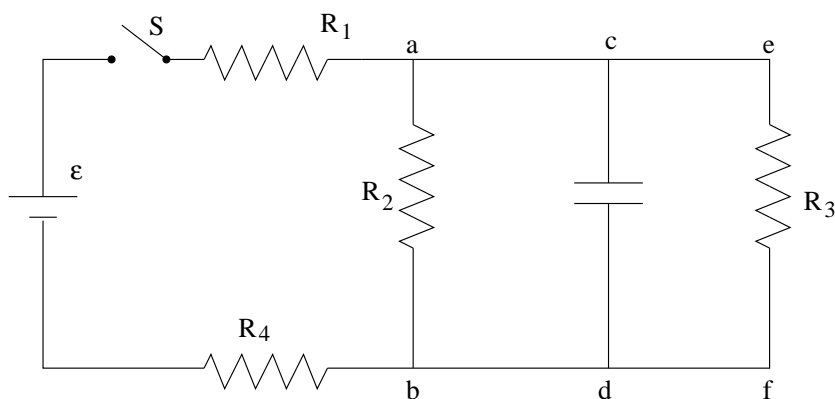


PHY6938 E & M Spring 99 and Fall 98

Note: hand in questions 1, 3, 5 and 6 as homework; we will work 2 and 4 in class on Tuesday February 27.


1. When switch S is closed, a current flows in the circuit which changes with time. Eventually, after a sufficiently long time, a steady state is reached in which all current is constant. Unless otherwise instructed, give all answers for this steady situation. For the circuit shown:




$$\begin{aligned}\epsilon &= 10 \text{ V} \\ R_1 &= R_4 = 500 \, \Omega \\ R_2 &= 6 \text{ k}\Omega \\ R_3 &= 1.2 \text{ k}\Omega \\ C &= 6 \, \mu\text{F}\end{aligned}$$

- What is the battery current?
- What is the potential difference between points a and b (i.e. $V_a - V_b$)?
- What is the potential difference between points c and d? Between e and f?
- If switch S is reopened after a long time, write the equation for the time dependence of the current in the section of the circuit containing the capacitor.

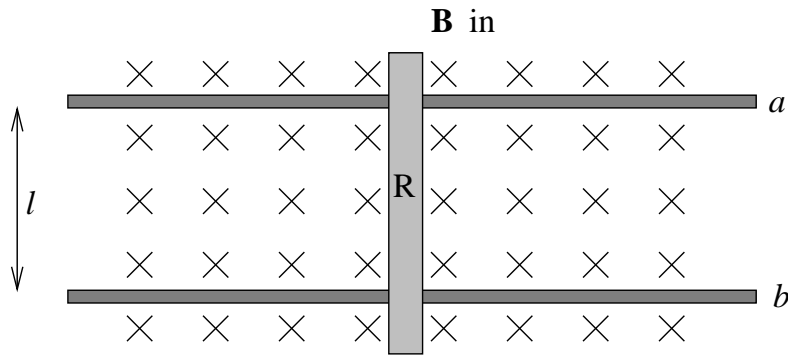2. In the figure below, the rod has a resistance R and mass M and the rails have negligible resistance. A capacitor with charge Q_0 and capacitance C is connected between points a and b such that the current in the rod is downward. The rod is at rest at time $t = 0$.




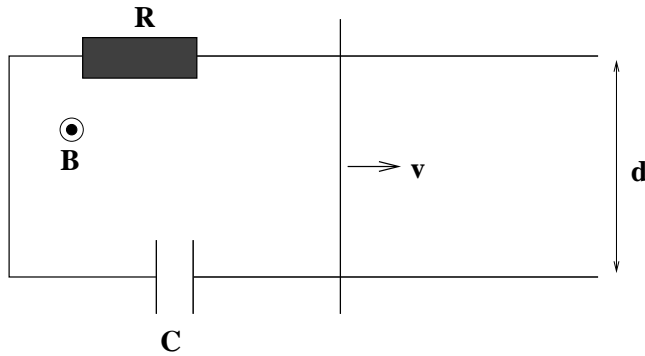- a) Write the equation of motion for the rod on the rails.
- b) Show that the terminal speed of the rod on the rails is related to the final charge on the capacitor.
- 3) A closed circuit loop consists of a resistor R , a capacitor C , two parallel conducting tracks a distance d apart, and a rigid wire that can slide along the tracks. A uniform magnetic field \mathbf{B} is applied perpendicular to the loop. Initially there is no current in the loop and the wire is at rest. At $t = 0$ it starts to move to the right with constant speed v , and it comes to a sudden stop at time $t = t_0$. Determine the charge on the capacitor for $t > 0$.



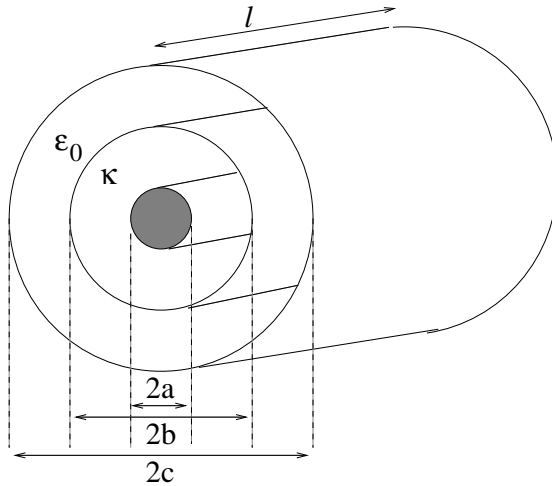- 4) A series AC circuit is operated at half its resonance frequency. The coil resistance is $40\ \Omega$, its inductance is $80\ \text{mH}$, and the capacitance is $0.4\ \mu\text{F}$.
 - a) What is the resonance frequency of the circuit?
 - b) What is the impedance of the circuit at half the resonance frequency?
 - c) What is the phase angle between the voltage and the current at half the resonance frequency?
 - d) What should the impedance of the source feeding this circuit be for maximum power transfer?
- 5) A coaxial capacitor of length l consists of an inner conductor of radius a , a cylindrical dielectric with dielectric constant k of inner radius a and outer radius b , and a shell of free

space of inner radius b and outer radius c . Beyond c is a conducting surface holding total charge q . The inner conductor carries charge $-q$.



- Find the radial component of the electric field \mathbf{E} in all regions of space.
 - Find the potential V in each region and the total potential across the capacitor (ignore all edge effects).
 - Find the capacitance.
 - Find the stored energy in the capacitor. Is the energy greater than or less than the energy stored in a similar capacitor with no dielectric?
- 6) What is the net electric force on charge q_1 ?

