



E & M Proficiency Exam, Spring 2001

Useful constants:

$$\begin{aligned}
 e &= 1.60 \times 10^{-19} \text{ C} \\
 hc &= 1240 \text{ eV} \cdot \text{nm} \\
 c &= 3.00 \times 10^8 \frac{\text{m}}{\text{s}} \\
 m_e &= 0.511 \frac{\text{MeV}}{c^2} \\
 k &= \frac{1}{4\pi\epsilon_0} = 8.99 \times 10^9 \frac{\text{Nm}^2}{\text{C}^2} \\
 \epsilon_0 &= 8.85 \times 10^{-12} \frac{\text{C}^2}{\text{Nm}^2}
 \end{aligned}$$

1. The two rails of a superconducting track are separated by a distance d . A conductor can slide along the track. The conductor, initially at rest, is pulled to the right by a constant force F . The friction force between the conductor and the track is directly proportional to its velocity with a proportionality constant α . The portion of the conductor between the rails has a resistance of R . The entire setup is in a uniform magnetic field \vec{B} as shown in the figure. The field \vec{B} points *into* the page.
 - (a) What is the direction of the induced current in the conductor?
 - (b) Determine the magnitude of the velocity of the conductor as a function of time.
 - (c) Determine the magnitude of the induced current as a function of time.
 - (d) Determine the terminal velocity of the conductor.

2. Consider a circuit consisting of a resistance $R = 6 \, \Omega$, an inductance $L = 0.5 \, \text{H}$ and a capacitance $C = 0.02 \, \text{F}$, all connected in series. A sinusoidal voltage $V(t) = V_0 \sin(\omega t)$ is applied to this LCR circuit.
- (a) What is the impedance of the circuit as a function of ω ?
 - (b) Find the resonance frequency.
 - (c) Assume now that $V_0 = 240 \, \text{V}$ and $\omega = 10 \, \text{rad/s}$. Assume that both the current and the charge vanish at $t = 0$. Obtain the charge on the capacitor, $Q(t)$, for these initial conditions.
3. A parallel plate capacitor with capacitance C is charged to a potential difference V and is then disconnected from the charging source. The capacitor has an area A and a plate separation z .
- (a) What is the force acting on the upper capacitor plate as a function of z ?
 - (b) Assume now that a glass plate of the same area A completely fills the space between the plates. The glass has a dielectric constant κ . How much work is required to pull the glass plate out of the capacitor?